

Ohm's Law Calculation Example

Example Question:

120V supplies a lamp that has a resistance of 192 ohms. What is the current flow in the circuit?

$$I = V/R$$

$$I = 120V/192 \text{ ohms}$$

Answer: $I = 0.625A$

