

Power Calculation Example

Example Question:

What is the power loss in watts for two conductors that carry 12A and have a voltage drop of 3.60V?

$$P = I \times V$$

$$P = 12A \times 3.60V$$

Answer: $P = 43.20W$

